

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Third Semester B.Tech Degree Regular and Supplementary Examination December 2022 (2019 Scheme)

Course Code: CST203**Course Name: Logic System Design**

Max. Marks: 100

Duration: 3 Hours

PART A**Answer all questions. Each question carries 3 marks**

Marks

- 1 Perform the mentioned base conversions for the following numbers. (3)
(i) $(563.8125)_{10}$ to binary (ii) $(78.89)_{10}$ to octal (iii) $(EC.4)_{16}$ to decimal
- 2 The 2's complement representation of a binary number is 10101100. (3)
(i) Determine its decimal value. (ii) Represent it in 1's complement form.
- 3 Prove that $x(x + y) = x$ using Boolean algebra postulates and rules. (3)
- 4 Find the number of possible unique Boolean functions which can be formed using n Boolean variables? Explain. (3)
- 5 Design an even parity code generator using XOR gates for a 4-bit code. (3)
- 6 Design an octal-to-binary encoder circuit using OR gates. (3)
- 7 Specify the characteristics table and characteristic equation of RS flip-flop. (3)
- 8 Differentiate synchronous counters and asynchronous counters. Give examples. (3)
- 9 Design a 4-bit shift register using D flipflops. (3)
- 10 Describe Read Only Memory with the help of a block diagram. (3)

PART B**Answer any one full question from each module. Each question carries 14 marks****Module 1**

- 11 a (i) Convert $(10111101.11100110)_2$ to octal and hexadecimal bases. (ii) (7)
Perform the binary operations 1101×110 and $10111 + 1101$
- b Convert the following decimal numbers to 8421 BCD and perform the operations. i) $528 + 374$ ii) $528 - 374$ (7)

- 12 a (i) Perform the binary subtraction $11011 - 1101$ using 1's and 2's complements and verify results by direct subtraction. (10)
- (ii) Perform the decimal subtraction $2210 - 3560$ using 9's and 10's complements and verify results by direct subtraction.
- b Add (i) Hexadecimal numbers B2A and 5C7 (ii) Octal numbers 763 and 456 (4)

Module 2

- 13 a The Exclusive-OR gate is represented by the Boolean algebra expression $AB' + A'B$. Using DeMorgan's theorem and other Boolean algebra rules/laws derive an expression for Exclusive-NOR gate. (5)
- b Simplify the function $f(A, B, C, D) = \sum(0,1,2,8,12,13,14) + d(3,5,10,15)$ with Karnaugh map. d(.) refers to don't care conditions. Implement the simplified function using NAND gates. (9)
- 14 a Simplify the following function and implement using NOR gates. Assume both normal and complement inputs are available. $f(x, y, z) = \sum(0,4,6)$ (6)
- b Express $F(x, y, z) = (xy + z)(y + xz)$ in both canonical forms. (8)

Module 3

- 15 a How does look-ahead carry reduce the carry propagation time in a binary parallel adder? Derive the Boolean functions for the carry outputs at different stages of a 4-bit look-ahead carry generator. (7)
- b Design a 4-bit BCD adder and draw the block diagram. (7)
- 16 a Design a full adder circuit using a decoder and external gates. (6)
- b Design a 3-bit Gray to binary code converter. (8)

Module 4

- 17 a With a circuit diagram, explain the working of master-slave JK flip-flop. (7)
- b Explain the working of 4-bit register with parallel load with the help of a diagram. (7)
- 18 a Design a 4-bit binary asynchronous counter using JK flipflops. Give the state diagram and logic diagram. (8)

- b Design a synchronous BCD Counter. Give the excitation table and circuit diagram. (6)

Module 5

- 19 a Describe the working of Programmable Logic Array (PLA) with a block diagram. (7)
- b Illustrate the algorithm for addition of 2's-complement numbers. State why 2's complement representation is preferred for binary arithmetic operations. (7)
- 20 a Design 4 bit Johnson counter and show its timing sequence. (8)
- b Explain the representation of floating point numbers. State the algorithm for floating point addition. (6)
